

21. A Describe the internal circuit of an operational amplifier with a neat diagram.

OR

B Explain the operational amplifier characteristics and its parameters.

22. A Describe the procedure for solving a second order differential equation. How are the initial conditions set up?

OR

B Draw and explain the operation of a triangular wave generator.

23. A Explain the second order low pass and high pass Butterworth filters.

OR

B Explain how the 555 timer works as a monostable multivibrator. Compare the theoretical and experimental value of the pulse width of the waveform obtained.

24. A Explain the working of IC 723 general purpose regulators.

OR

B Explain the working of a 4-bit R- 2R Ladder D/A converter with a neat diagram.

25. A Explain the working of a universal shift register using IC 74194.

OR

B Explain JK flip flop. How will you construct JK flip flop from SR flip flop.

Four Pages
S. No. 70713

4/12/23
23PPHCT03

Reg. No.									
----------	--	--	--	--	--	--	--	--	--

END SEMESTER EXAMINATION NOV/DEC-2023

First Semester

M.Sc Physics

CORE PAPER III – LINEAR AND DIGITAL IC'S AND APPLICATIONS

Time: Three Hours

Maximum: 75 marks

SECTION A – (15 x 1 = 15 marks)

ANSWER ALL QUESTIONS

- The output impedance of an ideal op amp is _____.
A infinity B one
C Zero D 75 ohms
- The voltage gain for non - inverting summing amplifier is _____.
A $A_{CL} = 1 - R_f / R_1$ B $A_{CL} = 1 + R_f / R_1$
C $A_{CL} = R_f / R_1$ D $A_{CL} = R_1 / R_f$
- The Op-Amp circuit, in which the output equals input and in phase is called as _____.
A voltage doubler B voltage rectifier
C voltage follower D average voltage
- Schmitt trigger is a special comparator which uses _____.
A negative feedback B positive feedback
C no feedback D negative and positive feedbacks
- _____ circuit is very useful in digital interfacing and pulse code modulation systems.
A Sample and hold B Log amplifier

- C Antilog amplifier D Instrumentation amplifier
6. Astable multivibrator is also known as _____ wave generator.
 A sine B saw tooth
 C square D Triangular
7. Determine the time period of a monostable 555 multivibrator.
 A $T = 0.33RC$ B $T = 1.1RC$
 C $T = 3RC$ D $T = RC$
8. Which characteristic of PLL is defined as the range of frequencies over which PLL can acquire lock with the input signal?
 A Free-running state B Pull-in time
 C Lock-in range D Capture range
9. Name the filter that has two stop bands.
 A Band-pass filter B High pass filter
 C Low pass filter D Band-reject filter
10. Drawback of counter type A/D converter is _____.
 A counter clears B high conversion time automatically
 C more complex D low speed
11. The series pass transistor in a linear IC voltage regulator is always in the _____ zone.
 A active B passive
 C cut-off D saturation
12. A 4 bit resistor divider D/A converter uses 80K ohm resistor for MSB, the resistor value used for LSB is _____.
 A 160 K ohm B 40 K ohm
 C 20 K ohm D 10 K ohm
13. The main advantage of CMOS is its _____.

- A high power rating B switching capability
 C small single operation D low power consumption
14. How many AND gates are required for the construction of 8:1 multiplexers?
 A 2 B 4
 C 6 D 8
15. A flip-flop which has only one input and which transfers the input data to the output on application of a clock pulse is called _____ flip flop.
 A SR B JK
 C D D T

SECTION B – (2 x 5 = 10 marks)
ANSWER ANY TWO QUESTIONS

16. Discuss the working of inverting amplifier.
17. Explain the working of Schmitt trigger using Op - Amp.
18. Explain the working voltage controlled oscillator using IC 566.
19. Explain the working of counter type A/D converter.
20. Explain the working of a CMOS NAND gate.

SECTION C – (5 x 10 = 50 marks)
ANSWER ALL QUESTIONS